



**DEPARTMENT OF ELECTRONICS AND COMMUNICATION
ENGINEERING**

**ST JOSEPH ENGINEERING COLLEGE
MANGALURU-575028**

Assignment-1
Simulation Assignment

Course Title	:	Digital System Design using Verilog
Laboratory Code	:	18EC644
Semester	:	VI
Student Name	:	Aaron Dsouza
USN	:	4SO20EC003
Section	:	A
Submitted to	:	Ms. Aswathi T
Submitted on	:	3-06-2023

1) Develop a Verilog model for a circuit that implements the following Boolean expressions:

a) $A + BC + \bar{B}D$

b) $\bar{B}C + B\bar{C} + \bar{D}$

a) $A + BC + \bar{B}D$

Solution:

➤ **Design code:**


```
module example_1 (y,a,b,c,d);  
output y;  
input a,b,c,d;  
assign y=a|(b&c)|(~b&d);  
endmodule
```

➤ **Test-bench code:**

```
module example_1_tb ();  
reg a,b,c,d;  
wire y;  
example_1 u0 (y,a,b,c,d);  
initial  
begin  
$monitor("a = %b, b = %b, c = %b, d = %b, y = %b", a, b, c, d, y);  
a=0; b=0; c=0; d=0;  
#5 a=0; b=0; c=0; d=1;  
#5 a=0; b=0; c=1; d=0;  
#5 a=0; b=0; c=1; d=1;  
#5 a=0; b=1; c=0; d=0;  
#5 a=0; b=1; c=0; d=1;  
#5 a=0; b=1; c=1; d=0;  
#5 a=0; b=1; c=1; d=1;  
#5 a=1; b=0; c=0; d=0;  
#5 a=1; b=0; c=0; d=1;  
#5 a=1; b=0; c=1; d=0;  
#5 a=1; b=0; c=1; d=1;  
#5 a=1; b=1; c=0; d=0;  
#5 a=1; b=1; c=0; d=1;  
#5 a=1; b=1; c=1; d=0;  
#5 a=1; b=1; c=1; d=1;  
end
```

```
#5 $finish;  
end  
endmodule
```

Output:

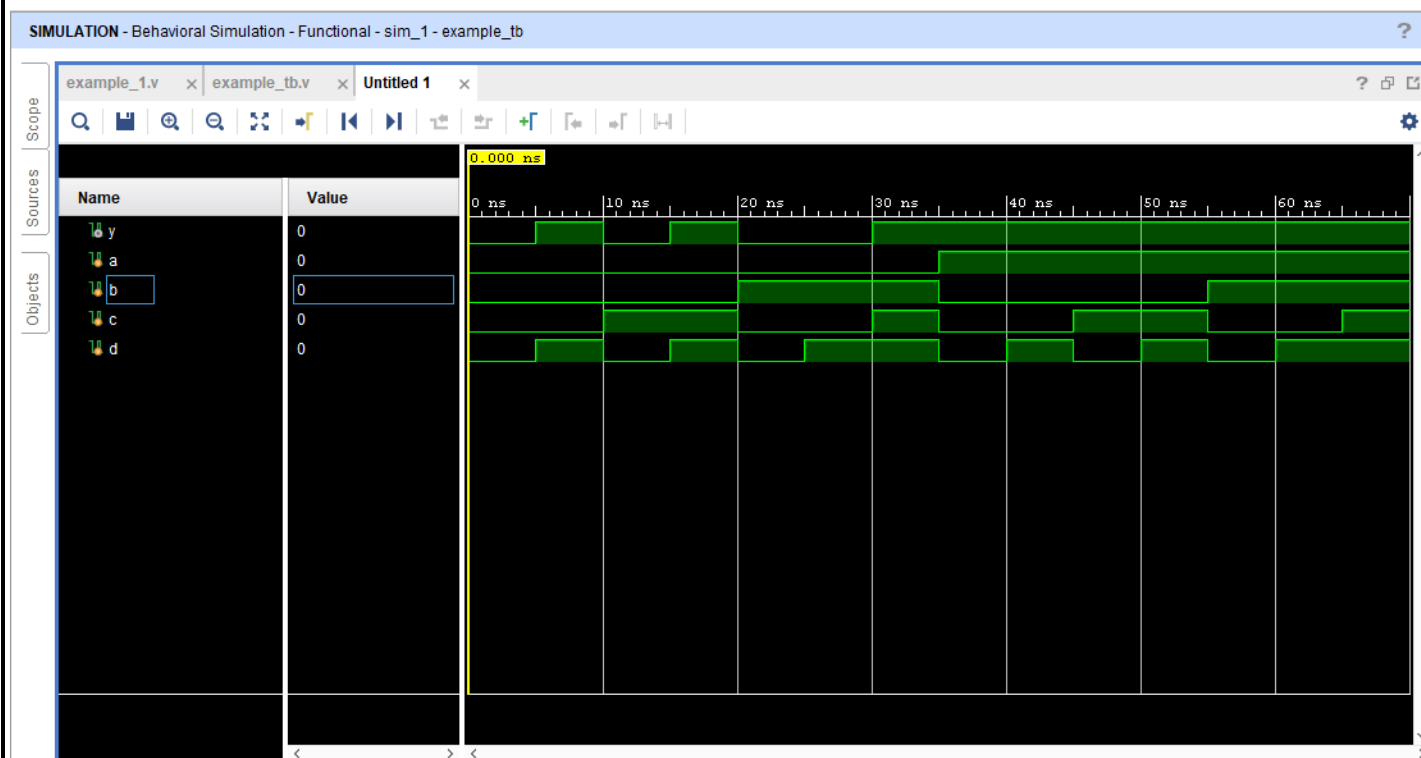

Verification:

```
[2023-05-27 00:30:41 EDT] iverilog '-Wall' design.sv testbench.sv && unbuffer vvp a.out
```

```
a = 0, b = 0, c = 0, d = 0, y = 0  
a = 0, b = 0, c = 0, d = 1, y = 1  
a = 0, b = 0, c = 1, d = 0, y = 0  
a = 0, b = 0, c = 1, d = 1, y = 1  
a = 0, b = 1, c = 0, d = 0, y = 0  
a = 0, b = 1, c = 0, d = 1, y = 0  
a = 0, b = 1, c = 1, d = 0, y = 1  
a = 0, b = 1, c = 1, d = 1, y = 1  
a = 1, b = 0, c = 0, d = 0, y = 1  
a = 1, b = 0, c = 0, d = 1, y = 1  
a = 1, b = 0, c = 1, d = 0, y = 1  
a = 1, b = 0, c = 1, d = 1, y = 1  
a = 1, b = 1, c = 0, d = 0, y = 1  
a = 1, b = 1, c = 0, d = 1, y = 1  
a = 1, b = 1, c = 1, d = 0, y = 1  
a = 1, b = 1, c = 1, d = 1, y = 1
```

Done

b) $\overline{B}C + B\overline{C} + \overline{D}$

Solution:


➤ **Design code:**

```
module example_1 (y,a,b,c,d);  
output y;  
input a,b,c,d;  
assign y=(~b&c)|(b&~c)|(~d);  
endmodule
```

➤ **Test-bench code:**

```
module example_1_tb ();  
reg a,b,c,d;  
wire y;  
example_1 u0 (y,a,b,c,d);  
initial  
begin  
$monitor ("a = %b, b = %b, c = %b, d = %b, y = %b", a, b, c, d, y);  
a=0; b=0; c=0; d=0;  
#5 a=0; b=0; c=0; d=1;  
#5 a=0; b=0; c=1; d=0;  
#5 a=0; b=0; c=1; d=1;  
#5 a=0; b=1; c=0; d=0;  
#5 a=0; b=1; c=0; d=1;  
#5 a=0; b=1; c=1; d=0;  
#5 a=0; b=1; c=1; d=1;  
#5 a=1; b=0; c=0; d=0;  
#5 a=1; b=0; c=0; d=1;  
#5 a=1; b=0; c=1; d=0;  
#5 a=1; b=0; c=1; d=1;  
#5 a=1; b=1; c=0; d=0;  
#5 a=1; b=1; c=0; d=1;  
#5 a=1; b=1; c=1; d=0;  
#5 a=1; b=1; c=1; d=1;  
#5 $finish;  
end  
endmodule
```

Output:

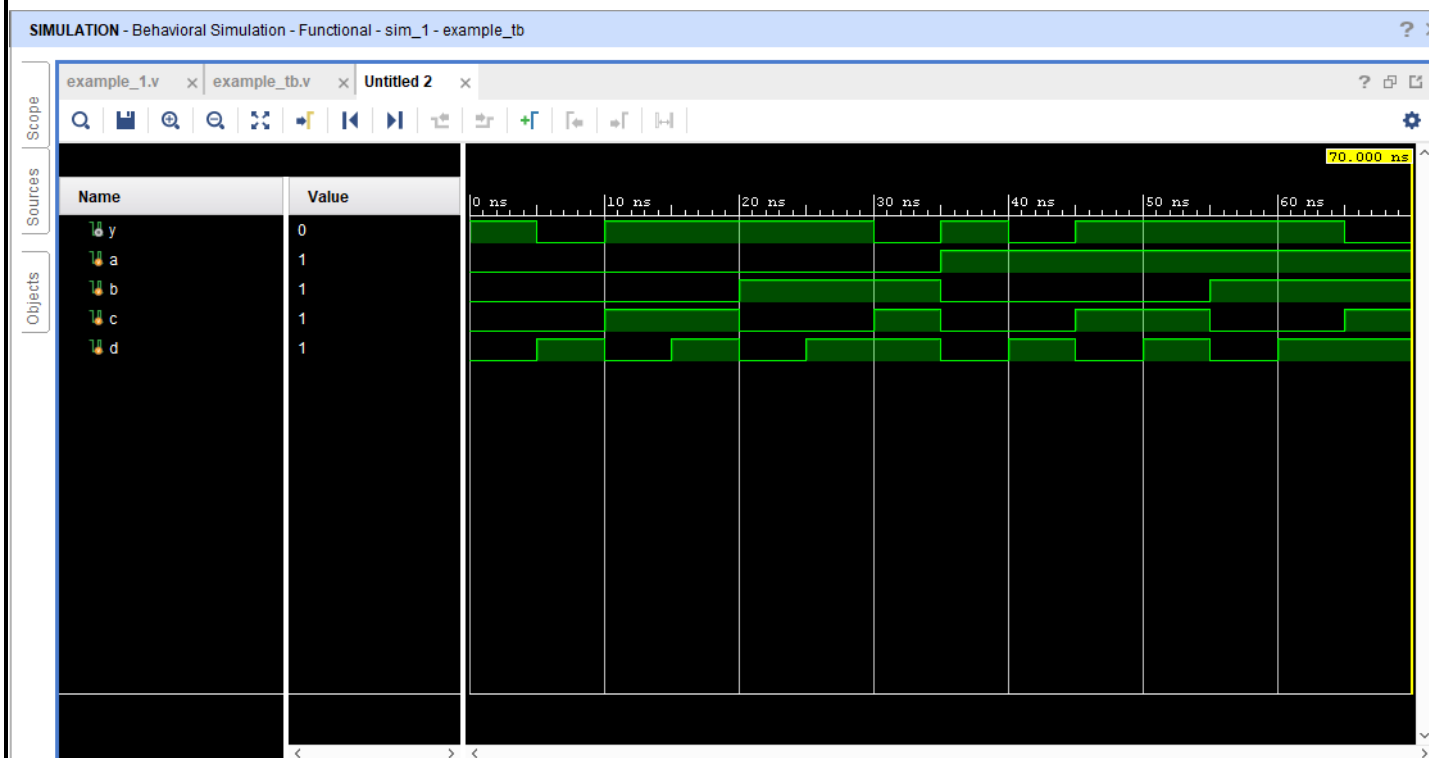


Verification:

```
[2023-05-27 00:37:21 EDT] iverilog '-wall' design.sv testbench.sv && unbuffer vvp a.out
```

```
a = 0, b = 0, c = 0, d = 0, y = 1
a = 0, b = 0, c = 0, d = 1, y = 0
a = 0, b = 0, c = 1, d = 0, y = 1
a = 0, b = 0, c = 1, d = 1, y = 1
a = 0, b = 1, c = 0, d = 0, y = 1
a = 0, b = 1, c = 0, d = 1, y = 1
a = 0, b = 1, c = 1, d = 0, y = 1
a = 0, b = 1, c = 1, d = 1, y = 0
a = 1, b = 0, c = 0, d = 0, y = 1
a = 1, b = 0, c = 0, d = 1, y = 0
a = 1, b = 0, c = 1, d = 0, y = 1
a = 1, b = 0, c = 1, d = 1, y = 1
a = 1, b = 1, c = 0, d = 0, y = 1
a = 1, b = 1, c = 0, d = 1, y = 1
a = 1, b = 1, c = 1, d = 0, y = 1
a = 1, b = 1, c = 1, d = 1, y = 0
```

Done

 2) Develop a Verilog model for the given combinational circuit that implements the three Boolean equations, representing part of the



Solution:

➤ **Design code:**

```

module indicator
(heater_on,cooler_on,fan_on>manual_heat,temp_low,auto_temp,temp_high>manual_co
ol>manual_fan);
output heater_on,cooler_on,fan_on;
input manual_heat,temp_low,auto_temp,temp_high>manual_cool>manual_fan;
wire w1,w2;
and a1(w1,temp_low,auto_temp);
and a2(w2,auto_temp,temp_high);
or o1(heater_on>manual_heat,w1);
or o2(cooler_on>manual_cool,w2);
or o3(fan_on,cooler_on,heater_on);
endmodule
  
```

➤ **Test-bench code:**

```

module indicator_tb;
reg manual_heat,temp_low,auto_temp,temp_high>manual_cool>manual_fan;
wire heater_on,cooler_on,fan_on;
indicator u0 (.heater_on(heater_on),.cooler_on(cooler_on),.fan_on(fan_on),
.manual_heat>manual_heat),.temp_low(temp_low),.auto_temp(auto_temp),
.temp_high(temp_high),.manual_cool>manual_cool),
.manual_fan>manual_fan));
Initial
begin
#10; $display("Input Values: manual_heat=%b,temp_low=%b,auto_temp=%b,
temp_high=%b>manual_cool=%b>manual_fan=%b",manual_heat,temp_low,
auto_temp,temp_high>manual_cool>manual_fan);
  
```

```
$monitor ("Output Signals: heater_on=%b, cooler_on=%b, fan_on=%b",heater_on,  
cooler_on, fan_on);
```

```
manual_heat = 0; temp_low = 0; auto_temp = 0; temp_high = 0; manual_cool = 0;  
manual_fan = 0;
```

```
#10;
```

```
manual_heat = 1; temp_low = 1; auto_temp = 0; temp_high = 0; manual_cool = 0;  
manual_fan = 0;
```

```
#10;
```

```
manual_heat = 0; temp_low = 0; auto_temp = 1; temp_high = 0; manual_cool = 0;  
manual_fan = 0;
```

```
#10;
```

```
manual_heat = 0; temp_low = 0; auto_temp = 1; temp_high = 1; manual_cool = 0;  
manual_fan = 0;
```

```
#10;
```

```
manual_heat = 0; temp_low = 0; auto_temp = 1; temp_high = 1; manual_cool = 1;  
manual_fan = 0;
```

```
#10;
```

```
manual_heat = 0; temp_low = 0; auto_temp = 1; temp_high = 1; manual_cool = 1;  
manual_fan = 1;
```

```
#10;
```

```
$finish;
```

```
end
```


```
endmodule
```

Output:

```
Input Values: manual_heat=x, temp_low=x, auto_temp=x, temp_high=x, manual  
_cool=x, manual_fan=x  
Output Signals: heater_on=0, cooler_on=0, fan_on=0  
Output Signals: heater_on=1, cooler_on=0, fan_on=1  
Output Signals: heater_on=0, cooler_on=0, fan_on=0  
Output Signals: heater_on=0, cooler_on=1, fan_on=1
```



Output Waveform:

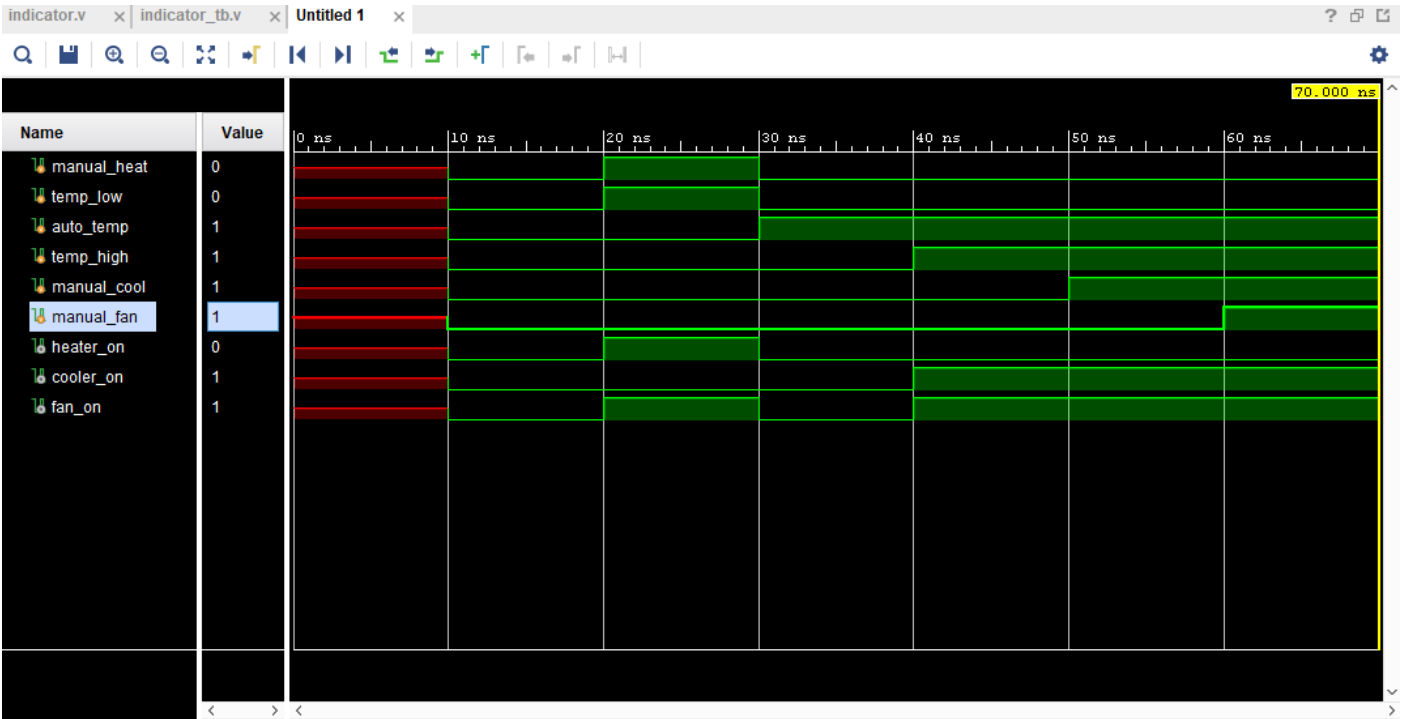

3) Develop a Verilog model for the following:

- a) 3 to 8-line Decoder
- b) 8 to 3-line Priority Encoder

a.)3 to 8-line Decoder:

Solution:

Design Code:

```
module encoder_8_3(a,y);
output reg [2:0]a;
input [7:0]y;
always@(y)
begin
case(y)
8'b00000001:a=3'b000;
8'b00000010:a=3'b001;
8'b00000100:a=3'b010;
8'b00001000:a=3'b011;
8'b00010000:a=3'b100;
8'b00100000:a=3'b101;
8'b01000000:a=3'b110;
8'b10000000:a=3'b111;
default:$display ("ERROR");
endcase
end
endmodule
```

Test-bench Code:

```
module encoder_tb();
reg[7:0]y;
wire[2:0]a;
encoder_8_3 u0(a,y);
initial
begin
y=8'b00000001;
#5 y=8'b00000010;
#5 y=8'b00000100;
#5 y=8'b00001000;
#5 y=8'b00010000;
#5 y=8'b00100000;
#5 y=8'b01000000;
```

```
#5 y=8'b10000000;  
#5 $finish;  
end  
endmodule
```

Output:



b) 8 to 3-line Priority Encoder:

Solution:

Design Code:


```
module encoder_8_3(a,y);  
output reg [2:0]a;  
input [7:0]y;  
always@(y)  
begin  
casex(y)  
8'b00000001:a=3'b000;  
8'b00000010:a=3'b001;  
8'b00000011:a=3'b010;  
8'b00000100:a=3'b011;  
8'b00000101:a=3'b100;  
8'b00000110:a=3'b101;  
8'b00000111:a=3'b110;  
8'b00001000:a=3'b111;  
end  
endmodule
```

```
default:$display ("ERROR");
endcase
end
endmodule
```

Test-bench Code:

```
module encoder_tb();
reg[7:0]y;
wire[2:0]a;
encoder_8_3 u0(a,y);
initial begin
y=8'b00000001;
#5 y=8'b0000001x;
#5 y=8'b000001xx;
#5 y=8'b00001xxx;
#5 y=8'b0001xxxx;
#5 y=8'b001xxxxx;
#5 y=8'b01xxxxxx;
#5 y=8'b1xxxxxxx;
#5 $finish;
end
endmodule
```

Output:

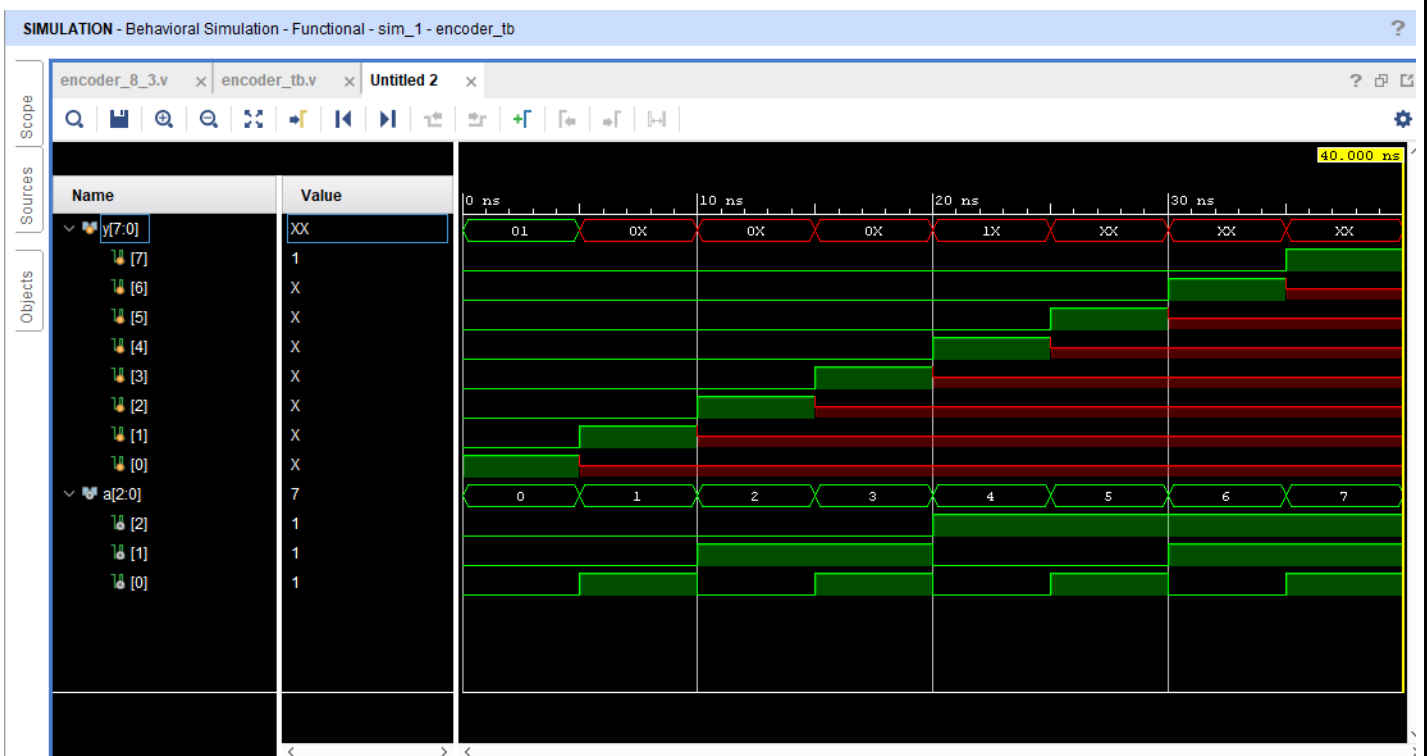

- 4) Implement the given Boolean expression using 4:1 MUX and develop a Verilog model the designed MUX.

$$Y = \sum m(0, 2, 6, 9, 11, 13)$$

Solution:

Binary Numbers:	Input A	Input B	Input C	Input D	Output Y
0	0	0	0	0	1
1	0	0	0	1	0
2	0	0	1	0	1
3	0	0	1	1	0
4	0	1	0	0	0
5	0	1	0	1	0
6	0	1	1	0	1
7	0	1	1	1	0
8	1	0	0	0	0
9	1	0	0	1	1
10	1	0	1	0	0
11	1	0	1	1	1
12	1	1	0	0	0
13	1	1	0	1	1
14	1	1	1	0	0
15	1	1	1	1	0

Simplification:

	I0	I1	I2	I3
00	0	4	8	12
01	1	5	9	13
10	2	6	10	14
11	3	7	11	15

➤ $I_0 = C'D' + CD'$

$= D'(C' + C)$

$I_0 = D'$


➤ $I_1 = CD'$

➤ $I_2 = C'D + CD$

$= D(C' + C)$

$I_2 = D$

➤ $I_3 = C'D$

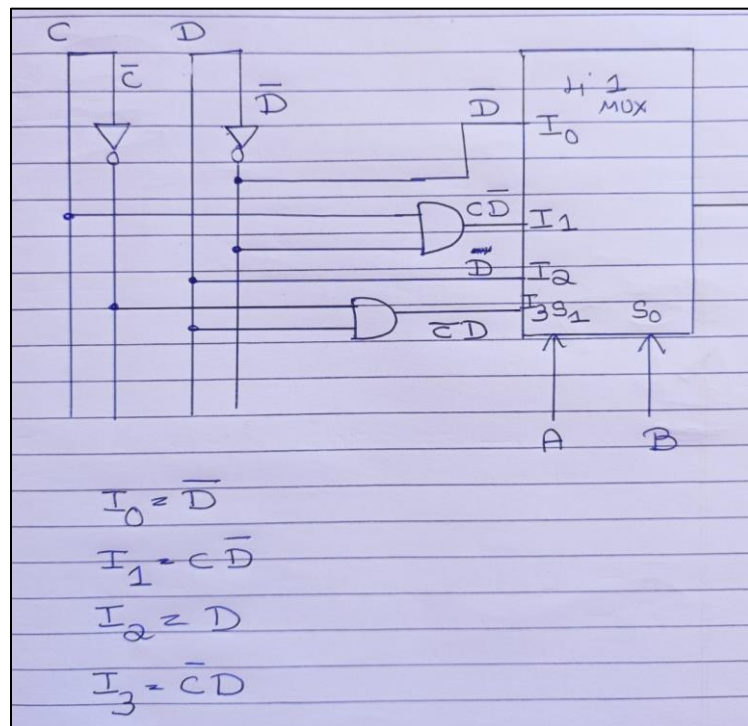

Design Code:

```

module mux4_1(y, sel,d,c);
input d, c;
input [1:0] sel;
output y;
reg y;
wire in_0, in_1, in_2, in_3;
  assign in_0 = ~d;
  assign in_1 = c & ~d;
  assign in_2 = d;
  assign in_3 = ~c & d;
  always @*

```

```
begin
case (sel)
    2'b00: y = in_0;
    2'b01: y = in_1;
    2'b10: y = in_2;
    2'b11: y = in_3;
    default: y = 1'bx;
endcase
end
endmodule
```

Test-bench Code:

```
module mux4_1_tb;
reg d, c;
reg [1:0] sel;
wire y;
mux4_1 uut (.d(d),.c(c),.sel(sel),.y(y));
initial
begin
    d = 0;
    c = 0;
    sel = 2'b00;
    #10;
    $display("d = %b, c = %b, sel = %b, y = %b", d, c, sel, y);
    d = 0;
    c = 1;
    sel = 2'b01;
    #10;
    $display("d = %b, c = %b, sel = %b, y = %b", d, c, sel, y);
    d = 1;
    c = 1;
    sel = 2'b10;
    #10;
    $display("d = %b, c = %b, sel = %b, y = %b", d, c, sel, y);
    d = 1;
    c = 0;
    sel = 2'b11;
    #10;
    $display("d = %b, c = %b, sel = %b, y = %b", d, c, sel, y);
    $finish;
end
endmodule
```

Output:

testbench.sv

1
2
3
4
5
6
7
8
9
10
11
12
13
14
15
16
17
18
19
20
21
22
23
24
25
26
27
28
29

```

module mux4_1_tb;
  reg d, c;
  reg [1:0] sel;
  wire y;
  mux4_1 uut (.d(d),.c(c),.sel(sel),.y(y));
  initial begin
    d = 0;
    c = 0;
    sel = 2'b00;
    #10;
    $display("d = %b, c = %b, sel = %b, y = %b", d, c, sel, y);
    d = 0;
    c = 1;
    sel = 2'b01;
    #10;
    $display("d = %b, c = %b, sel = %b, y = %b", d, c, sel, y);
    d = 1;
    c = 1;
    sel = 2'b10;
    #10;
    $display("d = %b, c = %b, sel = %b, y = %b", d, c, sel, y);
    d = 1;
    c = 0;
    sel = 2'b11;
    #10;
    $display("d = %b, c = %b, sel = %b, y = %b", d, c, sel, y);
    $finish;
  end
endmodule

```

design.sv

1
2
3
4
5
6
7
8
9
10
11
12
13
14
15
16
17
18
19
20
21
22

```

module mux4_1(y, sel,d,c);
  input d, c;
  input [1:0] sel;
  output y;
  reg y;

  wire in_0, in_1, in_2, in_3;
  assign in_0 = ~d;
  assign in_1 = c & ~d;
  assign in_2 = d;
  assign in_3 = ~c & d;

  always @* begin
    case (sel)
      2'b00: y = in_0;
      2'b01: y = in_1;
      2'b10: y = in_2;
      2'b11: y = in_3;
      default: y = 1'bx;
    endcase
  end
endmodule

```

Log
Share

[2023-06-03 04:36:05 EDT] iverilog '-wall' design.sv testbench.sv && unbuffer vvp a.out
d = 0, c = 0, sel = 00, y = 1
d = 0, c = 1, sel = 01, y = 1
d = 1, c = 1, sel = 10, y = 1
d = 1, c = 0, sel = 11, y = 1
Done

Output Waveform:

